Observations :

When O/P is open ckt. $I_2 = 0$				When I/P is open ckt. $I_1 = 0$			
$V_1$ (V)	$V_2$ (V)	$I_1$ (mA)	$Z_{11} = \frac{V_1}{I_1}$	$V_1$ (V)	$V_2$ (V)	$I_2$ (mA)	$Z_{21} = \frac{V_1}{I_2}$
5	2.5	2	2.5	1.25	2.5	5	2
10	4.5	5	2	0.9	4.5	10	5
12.5	5.5	6	2.083	0.916	6.0	12.5	6

$$Z = \begin{bmatrix} 2.194 & 1.022 \\ 1.022 & 2.194 \end{bmatrix}$$

Expt. No. 1

Experiment -1

\* AIM: To calculate and verify 'Z' & 'Y' parameters of two-port network.

\* Apparatus Required: power supply, bread board, three resistors, connecting leads, voltmeter, ammeter, etc.

\* 'Z' Parameters :

•) Brief theory: In Z parameters of a two-port, the input & output voltages  $V_1$  &  $V_2$  can be expressed in terms of input & output currents  $I_1$  &  $I_2$ . Out of four variables ( $V_1$ ,  $V_2$ ,  $I_1$ ,  $I_2$ ),  $V_1$  &  $V_2$  are dependent variables and  $I_1$  &  $I_2$  are independent.

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad (1)$$


$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad (2)$$

Here,  $Z_{11}$  &  $Z_{22}$  are input & output driving point impedances while  $Z_{12}$  &  $Z_{21}$  are reverse & forward transfer impedances.

•) Procedure:

1. Connect the variable voltage to port 1 & keep port 2 open circuit i.e.  $I_2 = 0$  as shown in figure. Set diff. voltages on  $V_1$  and measure  $V_1$ ,  $V_2$  and  $I_1$  for each setting and tabulate  $Z_{11}$  &  $Z_{21}$ .
2. Connect the variable voltage to port 2 & keep port 1 open circuit i.e.  $I_1 = 0$  as shown in figure. Set diff.

Teacher's Signature \_\_\_\_\_

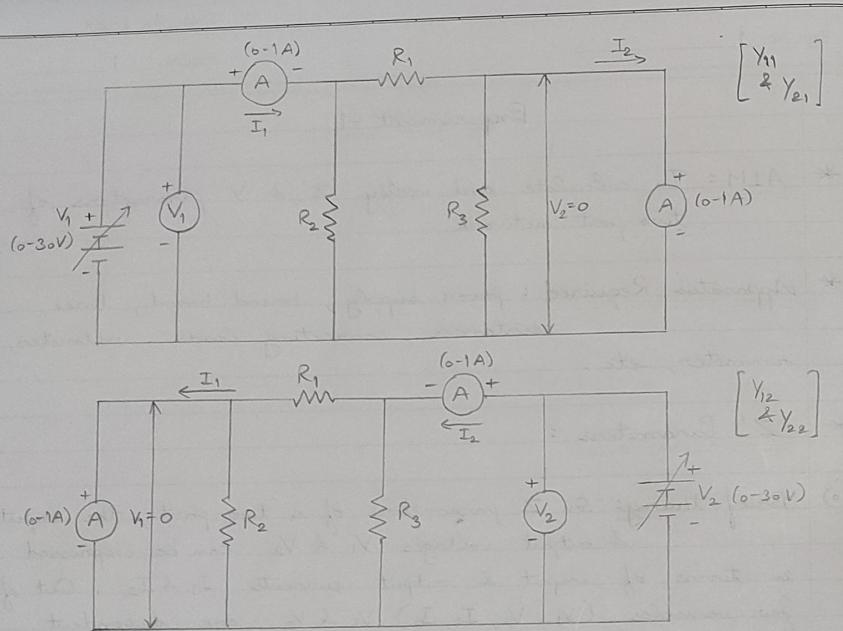Observations:When O/P is open ckt. V<sub>2</sub> = 0When I/P is open ckt. V<sub>1</sub> = 0

V <sub>1</sub> (V)	I <sub>1</sub> (mA)	I <sub>2</sub> (mA)	Y <sub>11</sub> = I <sub>1</sub> /V <sub>1</sub> (Ω)	Y <sub>21</sub> = I <sub>2</sub> /V <sub>1</sub> (Ω)	V <sub>2</sub> (V)	I <sub>1</sub> (mA)	I <sub>2</sub> (mA)	Y <sub>12</sub> = I <sub>1</sub> /V <sub>2</sub> (S)	Y <sub>22</sub> = I <sub>2</sub> /V <sub>2</sub> (S)
5	12	5	2.4	1	5	5	11	1	2.2
10	24	11	2.4	1.1	10	11	22	1.1	2.2
12.5	30	14	2.4	1.12	12.5	14	27	1.12	2.16

$$Z = \begin{bmatrix} 2.4 & 1.073 \\ 1.073 & 2.189 \end{bmatrix}$$

voltages at V<sub>2</sub> and measure V<sub>2</sub>, V<sub>1</sub>, I<sub>2</sub> for each setting and tabulate Z<sub>12</sub> & Z<sub>22</sub>.

\* 'Y' Parameters :

- ) Brief Theory: In Y-parameters of a two port, the input & output currents I<sub>1</sub> & I<sub>2</sub> can be expressed in terms of input & output voltages V<sub>1</sub> & V<sub>2</sub>. Out of 4 variables (I<sub>1</sub>, I<sub>2</sub>, V<sub>1</sub>, V<sub>2</sub>), I<sub>1</sub> & I<sub>2</sub> are dependent and V<sub>1</sub> & V<sub>2</sub> are independent.

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad (1)$$


$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad (2)$$

Here, Y<sub>11</sub> & Y<sub>22</sub> are the input & output driving point admittances while Y<sub>12</sub> & Y<sub>21</sub> are the reverse & forward transfer admittances.


\*) Procedure :

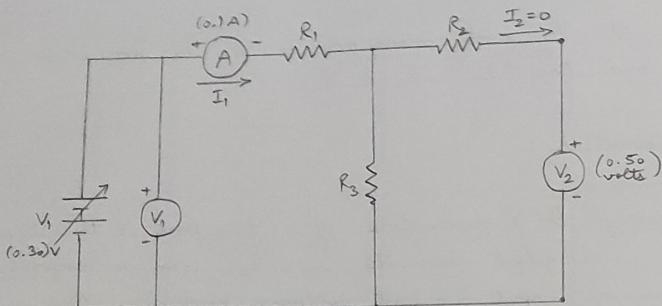1. Connect the variable voltage to port 1 and keep port 2 short i.e. V<sub>2</sub> = 0. Set diff. voltages on V<sub>1</sub> & measure V<sub>1</sub>, I<sub>1</sub> and I<sub>2</sub> for each setting and tabulate Y<sub>11</sub> & Y<sub>12</sub>.
2. Connect the variable voltage to port 2 and keep port 1 short i.e. V<sub>1</sub> = 0. Set diff. voltages on V<sub>2</sub> & measure V<sub>2</sub>, I<sub>1</sub>, I<sub>2</sub> for each setting and tabulate Y<sub>21</sub> & Y<sub>22</sub>.

\* Result : The Z & Y parameters of the two port network has been calculated and verified.



Circuit for determining ABCD.

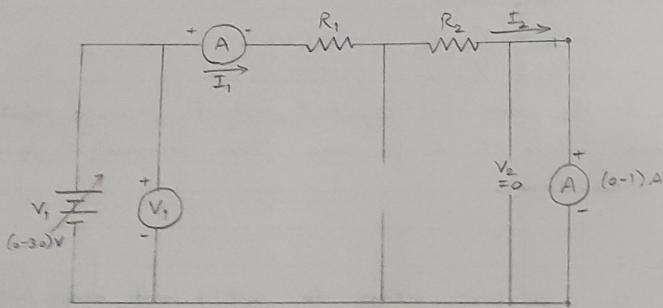

Circuit for determining B&amp;D.

Experiment - 2

\* AIM: To calculate and verify 'ABCD' parameters of two-port network.

\* Apparatus required: power supply, bread board, resistances, connecting leads, voltmeter, ammeter etc.

\* Theory: ABCD parameters are widely used in analysis of power transmission engineering where they are termed as "Circuit Parameters". ABCD parameters are also known as "Transmission Parameters". In these parameters, the voltage & current at the sending end terminals can be expressed in terms of voltage & current at the receiving end. Thus,

$$V_1 = AV_2 + B(-I_2)$$

$$\text{&} I_1 = C V_2 + D(-I_2)$$

Here, "A" is called reverse voltage ratio, "B" is called transfer impedance, "C" is called transfer admittance & "D" is called reverse current ratio.

Procedure :

1. Connect the variable voltage to port 1 and keep the port 2 open circuit i.e.  $I_2 = 0$  as shown. Set different voltages on  $V_1$  & measure  $V_1, V_2, I_1$  for each setting and tabulate ABC.
2. Connect the variable voltage to port 1 and keep port 2 short circuit i.e.  $V_2 = 0$ . At diff. voltages at  $V_1$  & measure  $V_2, I_2, I_1$  for each setting and tabulate B&D.

## \* Observations Table:

When O/P is open circ. $I_2 = 0$					When O/P is short circ. $V_2 = 0$				
$V_1(V)$	$V_2(V)$	$I_1(\text{mA})$	$A = V_1/V_2$	$C = I_1/I_2$ ( $\text{mV}$ )	$V_1(V)$	$I_1(\text{mA})$	$I_2(\text{mA})$	$B = V_1/I_2$ ( $\text{mV}$ )	$D = I_1/I_2$
5	2	4	2.5	2	5	3	1	-5	-3
10	4.5	5	2.22	1.11	10	6	2	-5	-3
12.5	5.5	6	2.27	1.091	12.5	8	3	-4.167	-2.667

$$A = 2.33$$

$$B = -4.722$$

$$C = 1.4003$$



$$D = 2.889$$

Expt. No. \_\_\_\_\_

## \* Precautions :

1. Make connections according to circuit diagram. Power supply should be switched off.
2. Connections should be tight.

\* Result : The ABCD-parameters of the two-port network has been calculated and verified.

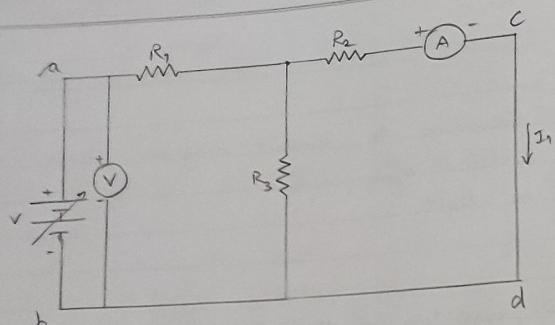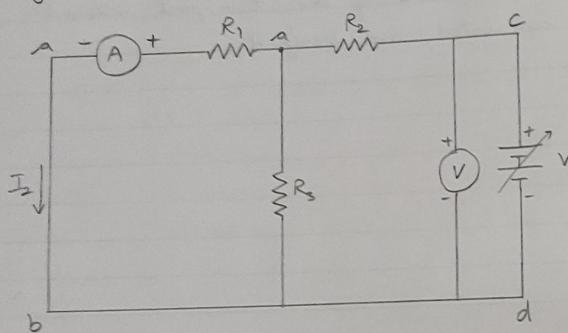Circuit for  
finding current  $I_1$ .Circuit for  
finding current  $I_2$ .**\* Observations Table:**

Input voltage $V$ (volts)	$I_1$ (mA)	$I_2$ (mA)	Error $I_1 - I_2$ (mA)
5	1	1	0
10	3	3	0
12.5	4	4	0

Expt. No. 3

Experiment - 3\* AIM: To verify Reciprocity theorem.\* Apparatus Required: power supply, bread board, three resistances, connecting leads, voltmeter, ammeter, etc.\* Theory: In any bilateral network, if a source of emf  $E$  in any branch produces a current  $I$  in any other branch, then the same emf  $E$  acting in the second branch would produce same current  $I$  in first branch.\* Procedure:

1. Connect the circuit as shown in figure.
2. Apply some voltage  $V$ .
3. Note down the ammeter reading as " $I_1$ ".
4. Inter change ammeter and voltage source and read the ammeter reading as " $I_2$ ".
5. Repeat the above procedure for different values of  $V$  and tabulate the values.
6.  $I_1$  should be equal to  $I_2$ .



\* Precautions:

1. Connect circuit elements as shown.
2. Avoid loose connections.
3. Take readings carefully & accurately.
4. Do not tamper the circuit elements.

\* Result:  $I_1 = I_2$ 

Teacher's Signature

Expt. No. 4

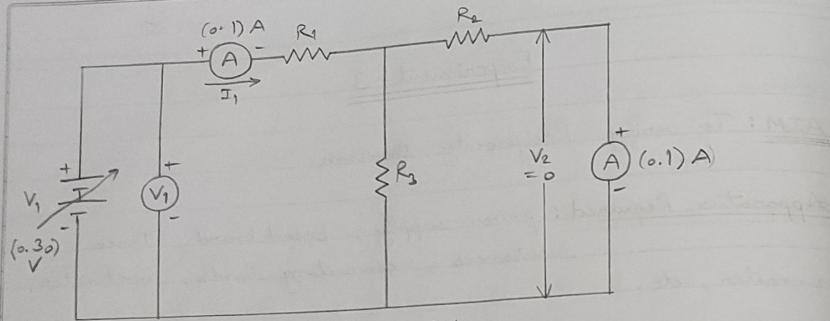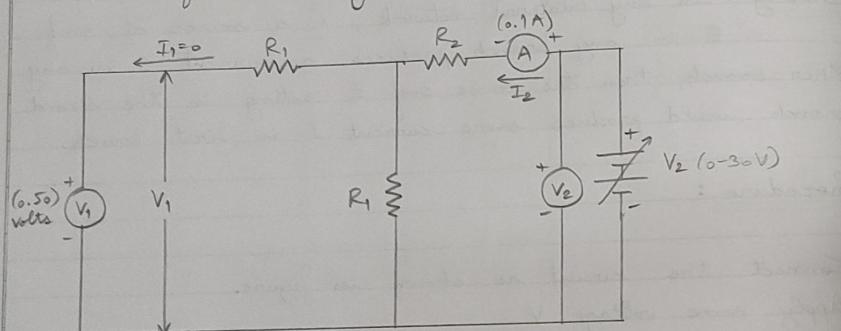Experiment - 4Circuit for determining  $h_{11}$  &  $h_{21}$ .Circuit for determining  $h_{12}$  &  $h_{22}$ .

\* AIM: To calculate and verify 'h' parameters of 2 port networks.

\* Apparatus Required: power supply, breadboard, 5 resistances, connecting leads, multimeter.

\* Theory: In 'h' parameters of a two port network, voltage of input port & current of output port are expressed in terms of current of input port and voltage of output port. Due to this reason, these parameters are called 'hybrid' parameters i.e. out of four variables ( $V_1$ ,  $V_2$ ,  $I_1$ ,  $I_2$ )  $V_1$  &  $I_2$  are dependent while  $V_2$  &  $I_1$  are independent. Thus,

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$h_{11}$  &  $h_{22}$  are input impedance & output admittance.

$h_{21}$  &  $h_{12}$  are forward current gain & reverse voltage gain.

\* Procedure:

1. Connect the variable voltage to port 1 & keep port 2 short circuit i.e.  $V_2=0$ . Set different voltages on  $V_1$  & measure  $V_1$ ,  $I_2$ ,  $I_1$  for each setting and tabulate  $h_{11}$  &  $h_{21}$ .
2. Connect the variable voltage to port 2 & keep port 1 open circuit i.e.  $I_1=0$ . Set different voltages on  $V_2$  & measure  $V_1$ ,  $V_2$ ,  $I_2$  for each setting and tabulate  $h_{12}$  &  $h_{22}$ .

\* Observations Table:

When O/P is short ckt. $V_2 = 0$					When I/P is open ckt. $I_1 = 0$				
$V_1$ (V)	$I_1$ (mA)	$I_2$ (mA)	$h_{11} = V_2/I_1$ ( $\approx$ )	$h_{21} = I_2/I_1$	$V_2$ (V)	$I_2$ (mA)	$V_1$ (V)	$h_{12} = V_1/V_2$	$h_{22} = I_2$
5	3	2	1.667	0.667	5	2	1.5	0.3	0.4
10	7	3	1.428	0.4281	10	5	3.5	0.35	0.5
12.5	9	4	1.389	0.444	12.5	7	5	0.4	0.56





$$h = \begin{bmatrix} 1.494 & 0.35 \\ 0.513 & 0.4367 \end{bmatrix}$$

Expt. No. \_\_\_\_\_

\* Precautions :

1. Make the connections properly. Power supply should be switched off.
2. Connections should be tight.
3. Note readings carefully.

\* Result : The h-parameters of 2-port network has been calculated & verified.

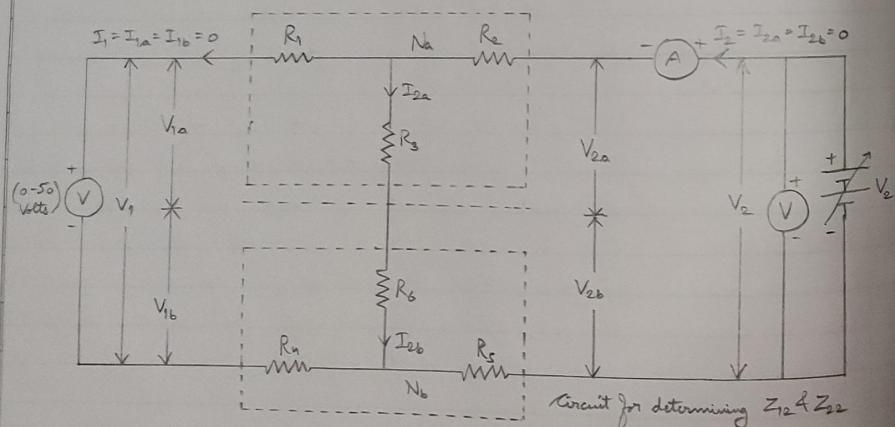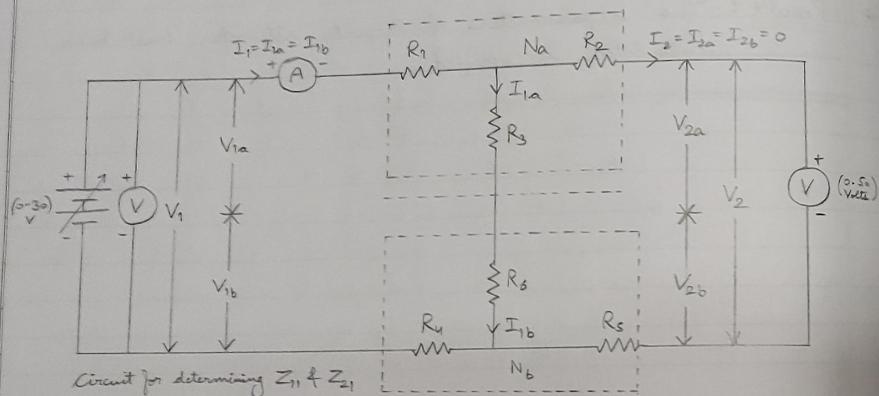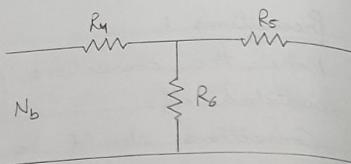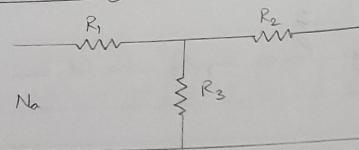Circuit Diagram:Experiment - 5

\* AIM: To determine the equivalent parameters of series connection of two port network.

\* Apparatus Required: power supply, bread board, resistances, connecting leads, multimeter etc.

\* Theory: Two 2-port networks are said to be connected in series if the corresponding ports are connected in series.

Let  $N_a$  be described by  $z$  parameters,  $N_b$  by  $z$  parameters and the overall two port network  $N$  by  $z$  parameters. Before the networks are interconnected, the relationship between voltages and currents for  $N$  are given by :

$$\begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} = \begin{bmatrix} Z_{11a} & Z_{12a} \\ Z_{21a} & Z_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix}$$

Similarly for the network  $N_b$ ,

$$\begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix} = \begin{bmatrix} Z_{11b} & Z_{12b} \\ Z_{21b} & Z_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$

In matrix form we can write,

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11a} + Z_{11b} & Z_{12a} + Z_{12b} \\ Z_{21a} + Z_{21b} & Z_{22a} + Z_{22b} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Observation Tables:

- When O/P is open circuit

$V_2$ (V)	$V_1$ (V)	$V_{1a}$ (V)	$V_{1b}$ (V)	$V_{2a}$ (V)	$V_{2b}$ (V)	$I_1 =$ $I_{1a} = I_{1b}$ (mA)	$Z_{11a} =$ $\frac{V_{1a}}{I_{1a}}$ ( $\Omega$ )	$Z_{11b} =$ $\frac{V_{1b}}{I_{1b}}$ ( $\Omega$ )	$Z_{21a} =$ $\frac{V_{2a}}{I_{1a}}$ ( $\Omega$ )	$Z_{21b} =$ $\frac{V_{2b}}{I_{1b}}$ ( $\Omega$ )	$Z_{11} =$ $\frac{V_1}{I_1}$ ( $\Omega$ )	$Z_{21} =$ $\frac{V_2}{I_1}$ ( $\Omega$ )
2.5	5	2.5	2.5	1.25	1.25	1	2.5	2.5	1.25	1.25	5	2.5
4.5	10	5	5	2.25	2.25	2.5	2	2	0.9	0.9	4	1.8
6	12.5	6.25	6.25	3	3	3	2.083	2.0837	0.916	1.034	4.1667	2

- When I/P is open circuit

$V_2$ (V)	$V_1$ (V)	$V_{1a}$ (V)	$V_{1b}$ (V)	$V_{2a}$ (V)	$V_{2b}$ (V)	$I_2 =$ $I_{2a} = I_{2b}$ (mA)	$Z_{22a} =$ $\frac{V_{2a}}{I_{2a}}$ ( $\Omega$ )	$Z_{22b} =$ $\frac{V_{2b}}{I_{2b}}$ ( $\Omega$ )	$Z_{12a} =$ $\frac{V_{1a}}{I_{2a}}$ ( $\Omega$ )	$Z_{12b} =$ $\frac{V_{1b}}{I_{2b}}$ ( $\Omega$ )	$Z_{12} =$ $\frac{V_1}{I_2}$ ( $\Omega$ )	$Z_{22} =$ $\frac{V_2}{I_2}$ ( $\Omega$ )
5	2.5	1.25	1.25	2.5	2.5	1	2.5	2.5	1.25	1.25	2.5	5
10	9.5	2.25	2.25	5	5	2.5	2	2	0.9	0.9	1.8	4
12.5	15.5	2.75	2.75	6.25	6.25	3	2.083	2.0837	0.9167	0.9167	4.1667	4.1667

$$Z = \begin{bmatrix} 4.3889 & 2.0443 \\ 2.1 & 4.3889 \end{bmatrix}$$

For the overall network N,

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Thus, the matrix of the two 2-port networks connected in series-series is equal to the sum of the z matrices of the individual networks,

$$[Z] = [Z_a] + [Z_b]$$

This result may be generalised for any number of 2-port networks connected in series. The overall z network matrix for the series-series connected 2-port networks is the sum of z matrices of the individual networks.

\* Procedure :

- Connect the circuit and switch 'ON' the experiment board.
- Open the output port & excite input port with a known voltage source  $V_s$  so that  $V_1 = V_s$  and  $I_2 = 0$ . We determine  $V_2, V_{1a}, V_{1b}, V_{2a}, V_{2b}, I_1$  to obtain  $Z_{11}, Z_{11a}, Z_{11b}, Z_{21}, Z_{21a}, Z_{21b}$ .
- Input port is open circuited and output port is excited with the same voltage source  $V_s$  so that  $V_2 = V_s$  &  $I_1 = 0$ . We determine  $V_1, V_{1a}, V_{1b}, V_{2a}, V_{2b}, I_2$  to obtain  $Z_{22}, Z_{22a}, Z_{22b}, Z_{12}, Z_{12a}, Z_{12b}$ .
- Switch OFF the supply after taking the readings.

Expt. No. \_\_\_\_\_

**\* Precautions :**

1. Make the connections according to the circuit diagram.  
Power supply should be switched off.
2. Connections should be tight.
3. Note the readings carefully.




**\* Result :**

$$Z_{11} = Z_{11a} + Z_{11b}$$

$$Z_{22} = Z_{22a} + Z_{22b}$$

$$Z_{12} = Z_{12a} + Z_{12b}$$

$$Z_{21} = Z_{21a} + Z_{21b}$$

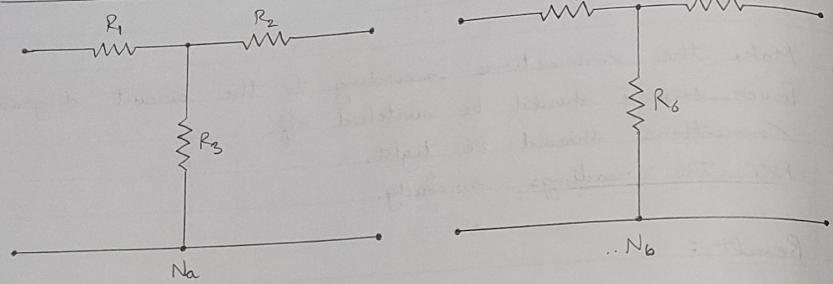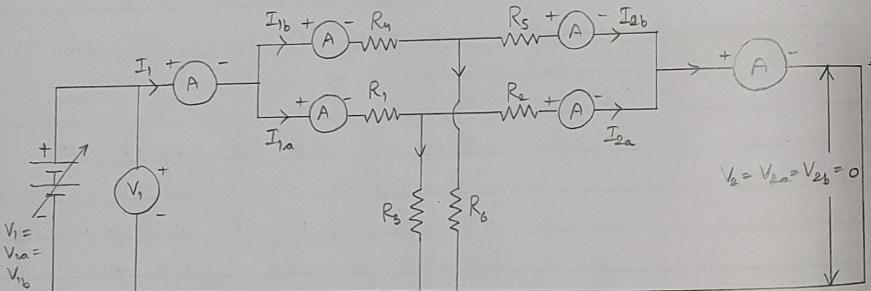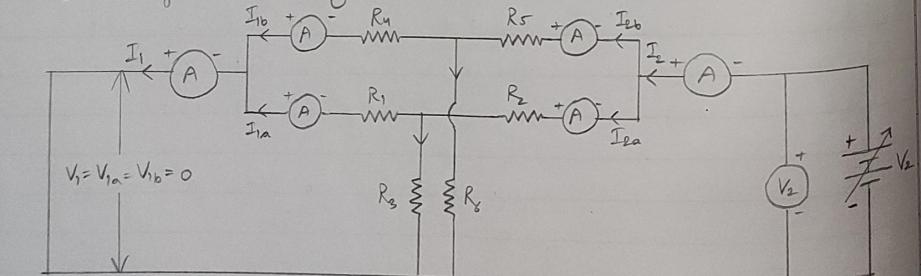Circuit Diagram:Circuit for determining  $Y_{11}$  &  $Y_{21}$ .Circuit for determining  $Y_{12}$  &  $Y_{22}$ .Experiment - 6

\* AIM: To determine equivalent parameters of parallel connection of two-port network.

\* Apparatus Required: power supply, bread board, 6 resistances, connecting leads, voltmeter, ammeter, etc.

\* Theory: The method of interconnecting two 2-port networks shown in figure is called a parallel-parallel connection of two ports because the corresponding ports of each network are connected in parallel. Let us find the parameters of the overall 2-port network N. Before the networks are interconnected, the network Na satisfies

$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} y_{11a} & y_{12a} \\ y_{21a} & y_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix}$$

Similarly, for the network Nb

$$\begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} y_{11b} & y_{12b} \\ y_{21b} & y_{22b} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$

In order to connect two networks Na & Nb in parallel, they must satisfy certain conditions. One test is performed at the output end and the other at the input end.

In matrix form we can write

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11a} + y_{11b} & y_{12a} + y_{12b} \\ y_{21a} + y_{21b} & y_{22a} + y_{22b} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

For the overall network N,

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Teacher's Signature

Observations Tables :

Output port short circuited,  $V_2 = 0$

$V_1 = V_{1b}$ $= V_{1a}$ (V)	$I_1$ (mA)	$I_2$ (mA)	$\gamma_{11} = I_1/V_1$ (25)	$\gamma_{21} = \frac{I_2}{V_1}$ (25)
5	23.5	10	4.7	2
10	48	22	4.8	2.2
12.5	~60	27.5	4.8	2.2

Input port short circuited,  $V_1 = 0$

$V_2 = V_{2b}$ $= V_{2a}$ (V)	$I_1$ (mA)	$I_2$ (mA)	$\gamma_{12} = I_2/V_2$ (25)	$\gamma_{22} = I_1/V_2$ (25)
5	11	22	4.4	2.2
10	22	43	4.3	2.2
12.5	28	~54	4.32	2.24

$$\gamma_a = \gamma_b = \begin{bmatrix} 2.4 & 1.073 \\ 1.073 & 2.1867 \end{bmatrix}$$

$$[\gamma_a] = [\gamma_{1a}] + [\gamma_{2a}]$$

$$Y_c = \begin{bmatrix} 4.7667 & 2.02133 \\ 2.02133 & 4.34 \end{bmatrix}$$

Thus, the  $\gamma$  matrix of the two 2-port networks connected in series-series is equal to the sum of the  $\gamma$  matrices of the individual networks,

$$[\gamma] = [\gamma_a] + [\gamma_b]$$

This result may be generalized for any no. of 2-port networks connected in parallel.

\* Procedure :

1. Connect the circuit as shown and switch 'ON' the experiment board.
2. Short the output port & excite input port with a known voltage source  $V_1$  so that  $V_1 = V_a$  &  $V_2 = 0$ . Use determine  $\gamma_{11}, \gamma_{12}, \gamma_{21}, \gamma_{22}, I_{1a}, I_{1b}, I_{2a}, I_{2b}, I_a, I_b$  to obtain  $\gamma_{1a}, \gamma_{1b}, \gamma_{2a}, \gamma_{2b}$ .

3. Input port is short circuited & output port is excited with the same voltage source  $V_2$  so that  $V_2 = V_b$  &  $I_1 = 0$ . We determine  $I_{1a}, I_{1b}, I_{2a}, I_{2b}, I_a, I_b, V_a$  to obtain  $\gamma_{12}, \gamma_{22}, \gamma_{1b}, \gamma_{2a}, \gamma_{2b}$ .
4. Switch OFF the supply after taking the readings.

\* Precautions :

1. Make connections according to the diagram. Power supply should be switched off.
2. Connections should be tight.
3. Note the readings carefully.

- \* Result : The  $\gamma$  parameters of parallel connection of 2-port networks have been determined.



Teacher's Signature

Experiment -7

\* AIM: To determine the 'ABCD' parameters of the cascade connection of two-part network.

\* Apparatus Required: power supply, breadboard, resistances, connecting leads, multimeter, etc.

Two cascaded networks and their equivalent network.

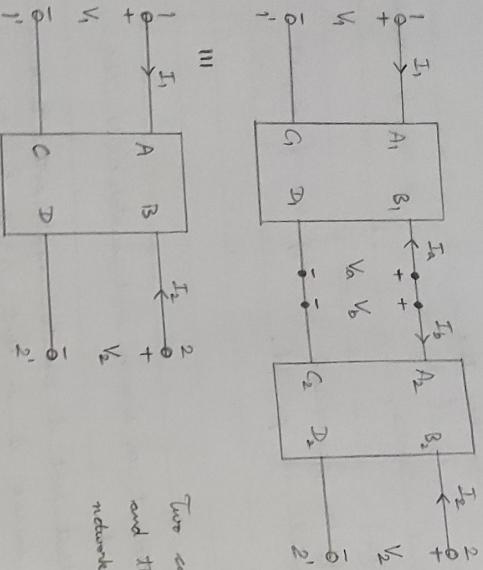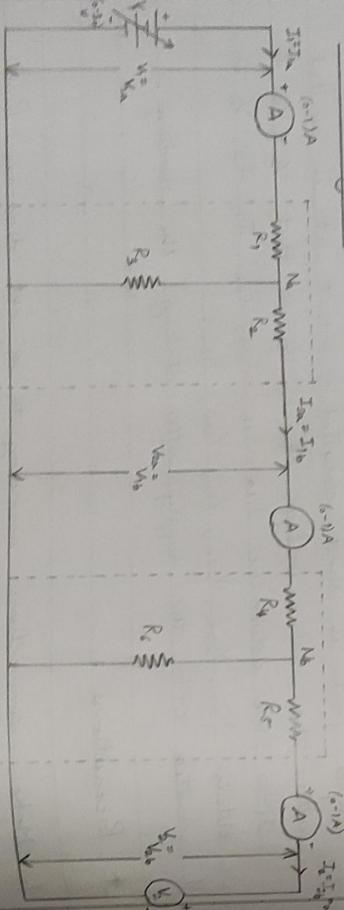\*) Circuit Diagram:

\* Theory: Two networks one said to be connected in cascade if the output port of one is the input port of the second as shown in fig.

The overall parameters for several two-port networks connected in cascade may conveniently be found using ABCD parameters. Figure shows two cascaded networks and their equivalent network. For the first network,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_a \\ -I_a \end{bmatrix}$$

For the second network,

$$\begin{bmatrix} V_b \\ I_b \end{bmatrix} = \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix} \begin{bmatrix} V_a \\ -I_a \end{bmatrix}$$

For the equivalent network,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_a \\ -I_a \end{bmatrix}$$


From figure,  $\begin{bmatrix} V_a \\ I_a \end{bmatrix} = \begin{bmatrix} V_b \\ I_b \end{bmatrix}$

Combination of above three equations gives

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} V_b \\ I_b \end{bmatrix}$$

Thus,

Result for determining ABCD

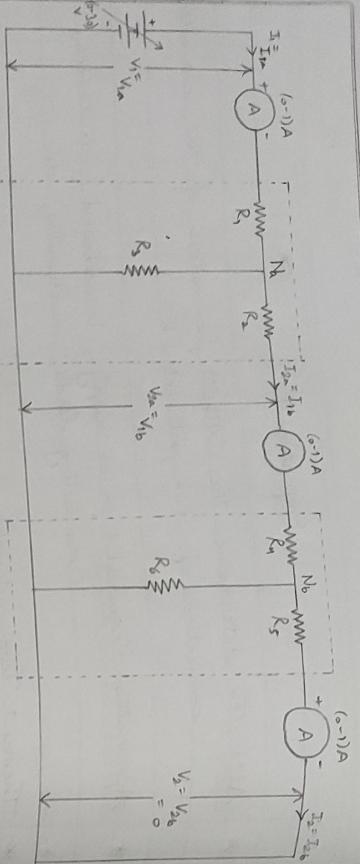

Circuit for determining B & D

Observation Table:

- When O/P is open circ.

$V_i = V_{1a}$	$V_o = V_{2b}$	$I_{1a} = I_{in}$	$A_1 = \frac{V_o}{V_i}$	$A_1 = \frac{V_{2b}}{V_{1a}}$	$C_1 = \frac{I_{1a}}{V_i}$	$C_1 = \frac{I_{in}}{V_{1a}}$
(V)	(V)	(mA)				

$V_i = V_{1a}$	$V_o = V_{2b}$	$I_{1a} = I_{in}$	$A_1 = \frac{V_o}{V_i}$	$A_1 = \frac{V_{2b}}{V_{1a}}$	$C_1 = \frac{I_{1a}}{V_i}$	$C_1 = \frac{I_{in}}{V_{1a}}$
(V)	(V)	(mA)				

- When O/P is short circ.

$V_i = V_{1a}$	$V_o = V_{2b}$	$I_{1a} = I_{in}$	$I_{2a} = I_{out}$	$B_1 = \frac{V_o}{I_{1a}}$	$B_2 = \frac{V_o}{I_{2a}}$	$D = \frac{I_{1a}}{I_{2a}}$	$D_1 = \frac{I_{1a}}{I_{2a}}$	$D_2 = \frac{I_{1a}}{I_{2a}}$
(V)	(V)	(mA)	(mA)					

\* Procedure :

- Connect the circuit as shown in fig. and switch ON the experiment board.
- Open the output port & excite input port with a known voltage source  $V_i$  so that  $V_i = V_o$  and  $I_2 = 0$  be determined to  $V_i(V_{1a})$ ,  $V_o(V_{2b})$ ,  $V_o(V_{2a})$ ,  $I_1(I_{1a})$ ,  $I_{in}(I_{in})$  to obtain  $A_1$ ,  $A_2$ ,  $C_1$ ,  $C_2$  as shown in fig.
- Input port is excited with the same voltage source  $V_i$  so that  $V_i = V_o$  & output port short circuited &  $V_o = 0$ . We determine  $V_i(V_{1a})$ ,  $V_o(V_{2a})$ ,  $I_1(I_{1a})$ ,  $I_{in}(I_{in})$ ,  $I_2(I_{2a})$  to obtain  $B_1$ ,  $B_2$ ,  $D_1$ ,  $D_2$  as shown in fig.
- Switch OFF the supply after taking the readings.

\* Precautions :

- Make the connections according to the circuit diagram.
- Power supply should be switched off.
- Connections should be tight.
- Note the readings carefully.

\* Result :

$$A = A_1 A_2 + B_1 C_2$$

$$B = A_1 B_2 + B_1 D_2$$

$$C = C_1 A_2 + D_1 C_2$$

$$D = C_1 B_2 + D_1 D_2$$